

# Circuit Complexity and Multiplicative Complexity of Boolean Functions


Alexander S. Kulikov  
joint work with Arist Kojevnikov

Steklov Institute of Mathematics at St. Petersburg

Franco-Russian workshop on Algorithms, complexity and applications  
14 June 2010
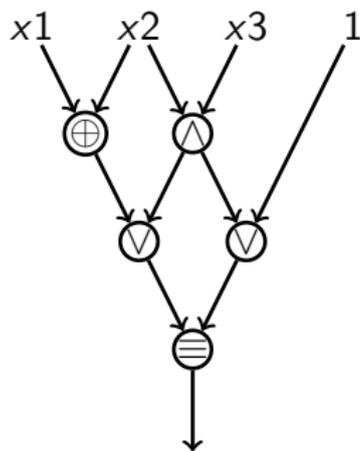
# Boolean Circuits

- inputs: propositional variables  $x_1, x_2, \dots, x_n$  and constants 0, 1
- gates: binary functions
- fan-out of a gate is unbounded



# Random Functions are Complex

# Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in  $n$  variables can be computed by circuits with  $t$  gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.

# Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in  $n$  variables can be computed by circuits with  $t$  gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.
- The number  $F(n, t)$  of circuits of size  $\leq t$  with  $n$  input variables does not exceed

$$(16(t + n + 2)^2)^t .$$

Each of  $t$  gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variable or a constant ( $\leq n + 2$  choices).

# Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in  $n$  variables can be computed by circuits with  $t$  gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.
- The number  $F(n, t)$  of circuits of size  $\leq t$  with  $n$  input variables does not exceed

$$(16(t + n + 2)^2)^t .$$

Each of  $t$  gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variable or a constant ( $\leq n + 2$  choices).

- For  $t = 2^n/(10n)$ ,  $F(n, t)$  is approximately  $2^{2^n/5}$ , which is  $\ll 2^{2^n}$ .

# Random Functions are Complex

- Shannon counting argument: count how many different Boolean functions in  $n$  variables can be computed by circuits with  $t$  gates and compare this number with the total number  $2^{2^n}$  of all Boolean functions.
- The number  $F(n, t)$  of circuits of size  $\leq t$  with  $n$  input variables does not exceed

$$(16(t + n + 2)^2)^t .$$

Each of  $t$  gates is assigned one of 16 possible binary Boolean functions that acts on two previous nodes, and each previous node can be either a previous gate ( $\leq t$  choices) or a variable or a constant ( $\leq n + 2$  choices).

- For  $t = 2^n/(10n)$ ,  $F(n, t)$  is approximately  $2^{2^n/5}$ , which is  $\ll 2^{2^n}$ .
- Thus, the circuit complexity of almost all Boolean functions on  $n$  variables is exponential in  $n$ . Still, we do not know any explicit function with super-linear circuit complexity.

# Known Lower Bounds

	circuit size	formula size
full binary basis $B_2$	$3n - o(n)$ [Blum]	$n^{2-o(1)}$ [Nechiporuk]
basis $U_2 = B_2 \setminus \{\oplus, \equiv\}$	$5n - o(n)$ [Iwama et al.]	$n^{3-o(1)}$ [Hastad]
monotone basis $M_2 = \{\vee, \wedge\}$	exponential [Razborov; Alon, Boppana; Andreev; Karchmer, Wigderson]	

# Explicit Functions

# Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.

# Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on  $n$  variables and take the first with circuit complexity at least  $2^n/(10n)$ .

# Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on  $n$  variables and take the first with circuit complexity at least  $2^n/(10n)$ .
- To avoid tricks like this one, we say that a function  $f$  is explicitly defined if  $f^{-1}(1)$  is in NP.

# Explicit Functions

- We are interested in **explicitly defined** Boolean functions of high circuit complexity.
- Not explicitly defined function of high circuit complexity: enumerate all Boolean functions on  $n$  variables and take the first with circuit complexity at least  $2^n/(10n)$ .
- To avoid tricks like this one, we say that a function  $f$  is explicitly defined if  $f^{-1}(1)$  is in NP.
- Usually, under a Boolean function  $f$  we actually understand an infinite sequence  $\{f_n \mid n = 1, 2, \dots\}$ .

# Known Lower Bounds for Circuits over $B_2$

## Known Lower Bounds

$2n - c$  [Kloss, Malyshev, 65]

$2n - c$  [Schnorr, 74]

$2.5n - o(n)$  [Paul, 77]

$2.5n - c$  [Stockmeyer, 77]

$3n - o(n)$  [Blum, 84]

# Known Lower Bounds for Circuits over $B_2$

## Known Lower Bounds

$2n - c$  [Kloss, Malyshev, 65]

$2n - c$  [Schnorr, 74]

$2.5n - o(n)$  [Paul, 77]

$2.5n - c$  [Stockmeyer, 77]

$3n - o(n)$  [Blum, 84]

## This Talk

# Known Lower Bounds for Circuits over $B_2$

## Known Lower Bounds

$2n - c$  [Kloss, Malyshev, 65]

$2n - c$  [Schnorr, 74]

$2.5n - o(n)$  [Paul, 77]

$2.5n - c$  [Stockmeyer, 77]

$3n - o(n)$  [Blum, 84]

## This Talk

- We present a proof of a  $7n/3 - c$  lower bound which is as simple as Schnorr's proof of  $2n - c$  lower bound.

# Known Lower Bounds for Circuits over $B_2$

## Known Lower Bounds

$2n - c$	[Kloss, Malyshev, 65]
$2n - c$	[Schnorr, 74]
$2.5n - o(n)$	[Paul, 77]
$2.5n - c$	[Stockmeyer, 77]
$3n - o(n)$	[Blum, 84]

## This Talk

- We present a proof of a  $7n/3 - c$  lower bound which is as simple as Schnorr's proof of  $2n - c$  lower bound.
- The key idea is a combined circuit complexity measure assigning different weight to gates of different types.

# Gate Elimination Method

## Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

# Gate Elimination Method

## Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

## The main idea

# Gate Elimination Method

## Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

## The main idea

- Take an optimal circuit for the function in question.

# Gate Elimination Method

## Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

## The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.

# Gate Elimination Method

## Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

## The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.

# Gate Elimination Method

## Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.

## The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.

# Gate Elimination Method

## Gate Elimination

All the proofs are based on the so-called **gate elimination method**. This is essentially the only known method for proving lower bounds on circuit complexity.


## The main idea

- Take an optimal circuit for the function in question.
- Setting some variables to constants obtain a subfunction of the same type (in order to proceed by induction) and eliminate several gates.
- A gate is eliminated if it computes a constant or a variable.
- By repeatedly applying this process, conclude that the original circuit must have had many gates.


## Remark

This method is very unlikely to produce non-linear lower bounds.


# Example

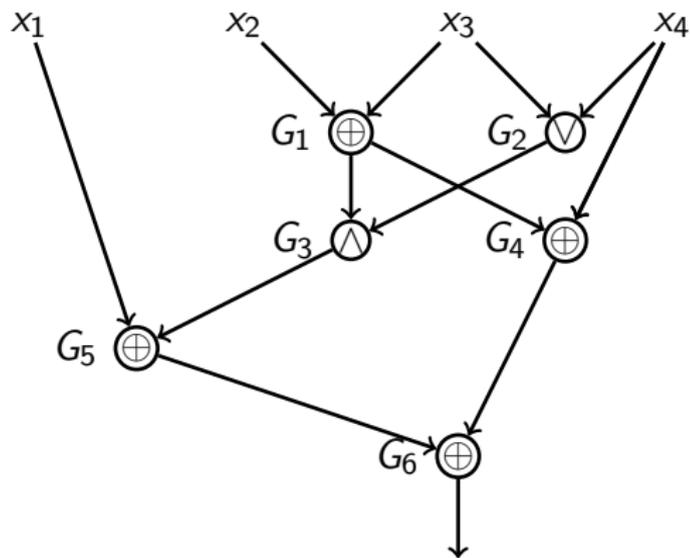

# Example

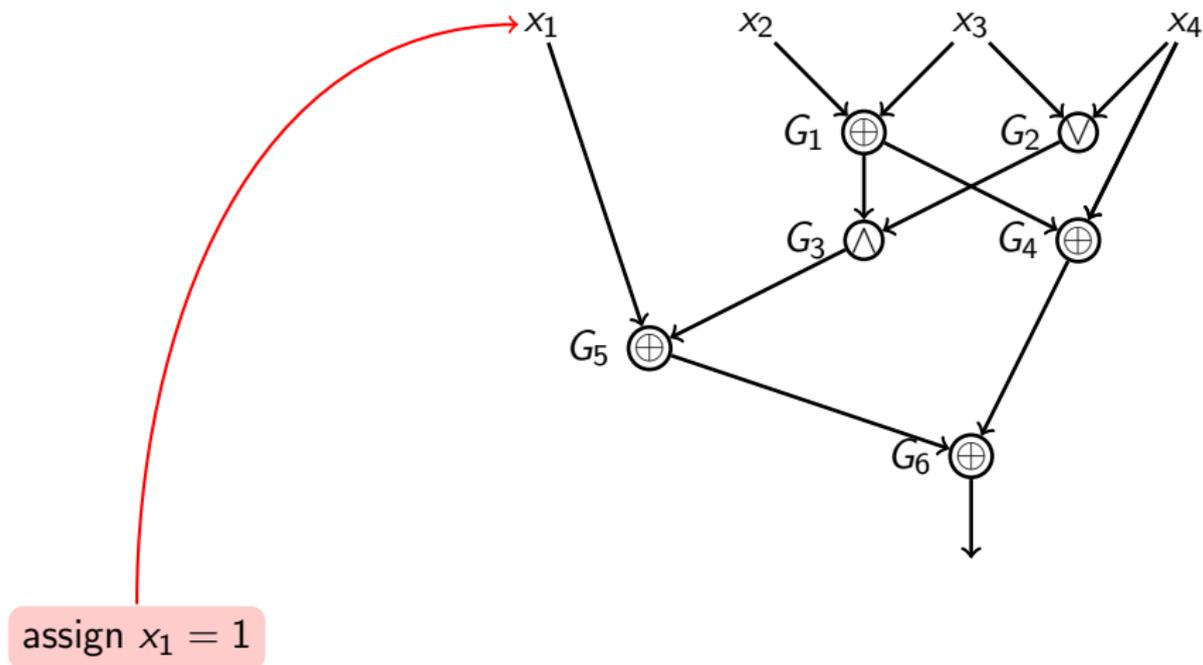


# Example

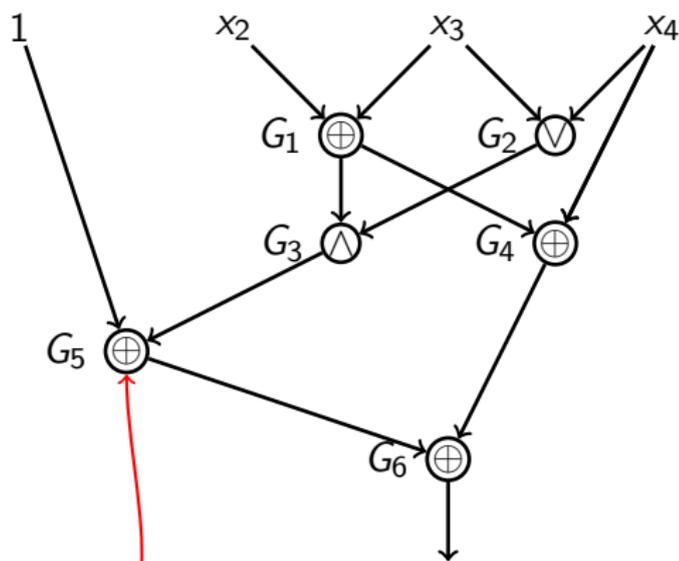


$G_5$  now computes  $G_3 \oplus 1 = \neg G_3$

# Example

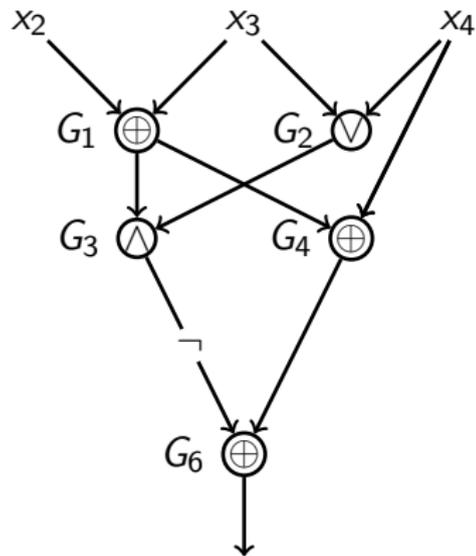


# Example

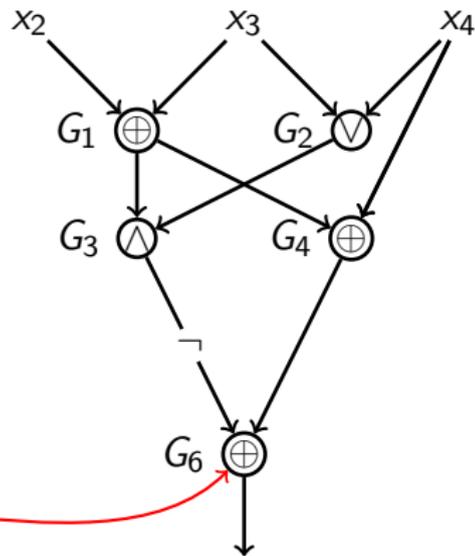


now we can change the binary function assigned to  $G_6$

# Example

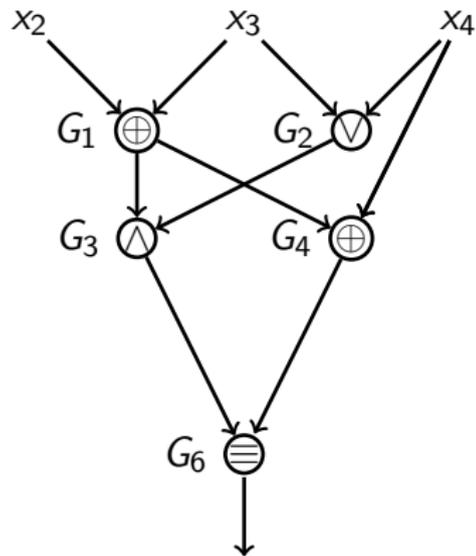


# Example

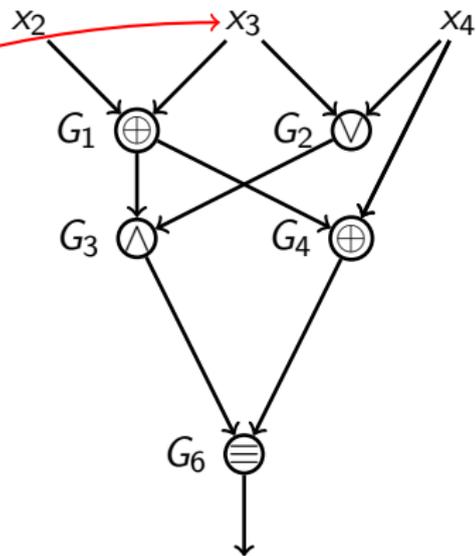


now assign  $x_3 = 0$

# Example

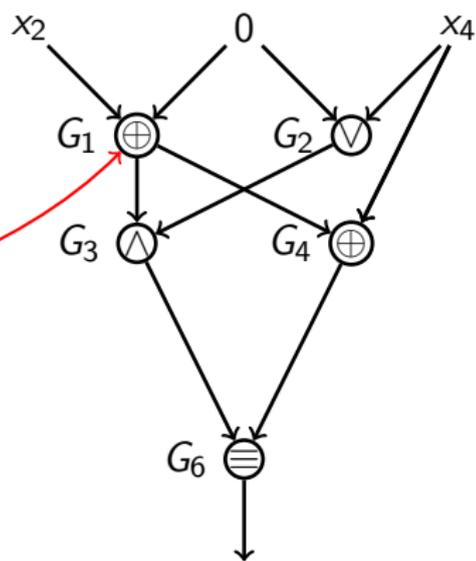


$G_1$  then is equal to  $x_2$

# Example

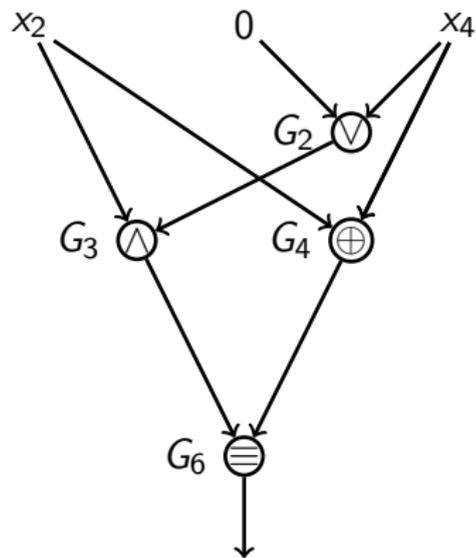


# Example

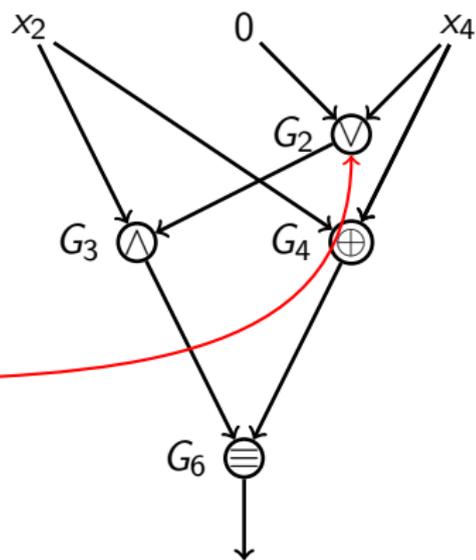

$$G_2 = x_4$$

# Example

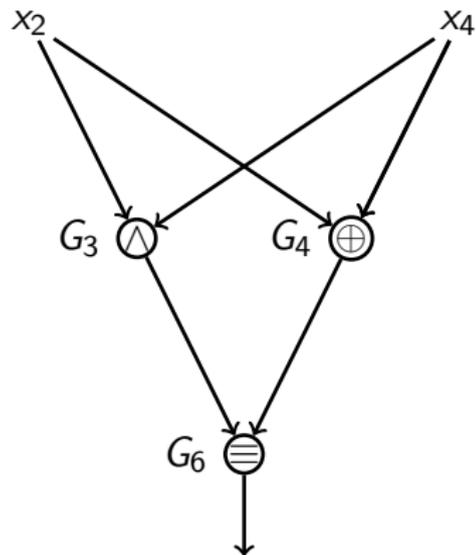

# The Class $Q_{2,3}^n$

## Definition

A function  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  belongs to the class  $Q_{2,3}^n$  if

# The Class $Q_{2,3}^n$

## Definition

A function  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  belongs to the class  $Q_{2,3}^n$  if

- 1 for all different  $i, j \in \{1, \dots, n\}$ , one obtains at least three different subfunctions by replacing  $x_i$  and  $x_j$  by constants;

# The Class $Q_{2,3}^n$

## Definition

A function  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  belongs to the class  $Q_{2,3}^n$  if

- 1 for all different  $i, j \in \{1, \dots, n\}$ , one obtains at least three different subfunctions by replacing  $x_i$  and  $x_j$  by constants;
- 2 for all  $i \in \{1, \dots, n\}$ , one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if  $n \geq 4$ ) by replacing  $x_i$  by any constant.

# The Class $Q_{2,3}^n$

## Definition

A function  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  belongs to the class  $Q_{2,3}^n$  if

- 1 for all different  $i, j \in \{1, \dots, n\}$ , one obtains at least three different subfunctions by replacing  $x_i$  and  $x_j$  by constants;
- 2 for all  $i \in \{1, \dots, n\}$ , one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if  $n \geq 4$ ) by replacing  $x_i$  by any constant.

## Modular functions

# The Class $Q_{2,3}^n$

## Definition

A function  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  belongs to the class  $Q_{2,3}^n$  if

- 1 for all different  $i, j \in \{1, \dots, n\}$ , one obtains at least three different subfunctions by replacing  $x_i$  and  $x_j$  by constants;
- 2 for all  $i \in \{1, \dots, n\}$ , one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if  $n \geq 4$ ) by replacing  $x_i$  by any constant.

## Modular functions

- Let  $\text{MOD}_{m,r}^n(x_1, \dots, x_n) = 1$  iff  $\sum_{i=1}^n x_i \equiv r \pmod{m}$ .

# The Class $Q_{2,3}^n$

## Definition

A function  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  belongs to the class  $Q_{2,3}^n$  if

- 1 for all different  $i, j \in \{1, \dots, n\}$ , one obtains at least three different subfunctions by replacing  $x_i$  and  $x_j$  by constants;
- 2 for all  $i \in \{1, \dots, n\}$ , one obtains a subfunction in  $Q_{2,3}^{n-1}$  (if  $n \geq 4$ ) by replacing  $x_i$  by any constant.

## Modular functions

- Let  $\text{MOD}_{m,r}^n(x_1, \dots, x_n) = 1$  iff  $\sum_{i=1}^n x_i \equiv r \pmod{m}$ .
- Then  $\text{MOD}_{3,r}^n, \text{MOD}_{4,r}^n \in Q_{2,3}^n$ , but  $\text{MOD}_{2,r}^n \notin Q_{2,3}^n$  (as one can only get  $\text{MOD}_{2,0}^{n-2}$  and  $\text{MOD}_{2,1}^{n-2}$  from  $\text{MOD}_{2,r}^n$  by fixing two constants).

# Schnorr's $2n$ Lower Bound

## Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \geq 2n - 8$ .

# Schnorr's $2n$ Lower Bound

## Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \geq 2n - 8$ .

## Proof

# Schnorr's $2n$ Lower Bound

## Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \geq 2n - 8$ .

## Proof

- Induction on  $n$ . If  $n \leq 4$ , then the statement is trivial.

# Schnorr's $2n$ Lower Bound

## Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \geq 2n - 8$ .

## Proof

- Induction on  $n$ . If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate  $Q$  which is fed by different variables  $x_i$  and  $x_j$  (they are different, since the circuit is optimal).

# Schnorr's $2n$ Lower Bound

## Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \geq 2n - 8$ .

## Proof

- Induction on  $n$ . If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate  $Q$  which is fed by different variables  $x_i$  and  $x_j$  (they are different, since the circuit is optimal).
- Note that  $Q = Q(x_i, x_j)$  can only take **two** values, 0 and 1, when  $x_i$  and  $x_j$  are fixed.

# Schnorr's $2n$ Lower Bound

## Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \geq 2n - 8$ .

## Proof

- Induction on  $n$ . If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate  $Q$  which is fed by different variables  $x_i$  and  $x_j$  (they are different, since the circuit is optimal).
- Note that  $Q = Q(x_i, x_j)$  can only take **two** values, 0 and 1, when  $x_i$  and  $x_j$  are fixed.
- Thus, either  $x_i$  or  $x_j$  fans out to another gate  $P$ .

# Schnorr's $2n$ Lower Bound

## Theorem

If  $f \in Q_{2,3}^n$ , then  $C(f) \geq 2n - 8$ .

## Proof

- Induction on  $n$ . If  $n \leq 4$ , then the statement is trivial.
- Consider an optimal circuit and its top gate  $Q$  which is fed by different variables  $x_i$  and  $x_j$  (they are different, since the circuit is optimal).
- Note that  $Q = Q(x_i, x_j)$  can only take **two** values, 0 and 1, when  $x_i$  and  $x_j$  are fixed.
- Thus, either  $x_i$  or  $x_j$  fans out to another gate  $P$ .
- By assigning this variable, we eliminate at least two gates and get a subfunction from  $Q_{2,3}^{n-1}$ . □

# AND-type Gates vs XOR-type Gates

## Binary functions

The set  $B_2$  of all binary functions contains 16 functions  $f(x, y)$ :

# AND-type Gates vs XOR-type Gates

## Binary functions

The set  $B_2$  of all binary functions contains 16 functions  $f(x, y)$ :

- 1 2 constants: 0, 1

# AND-type Gates vs XOR-type Gates

## Binary functions

The set  $B_2$  of all binary functions contains 16 functions  $f(x, y)$ :

- 1 2 constants: 0, 1
- 2 4 degenerate functions:  $x$ ,  $\bar{x}$ ,  $y$ ,  $\bar{y}$ .

# AND-type Gates vs XOR-type Gates

## Binary functions

The set  $B_2$  of all binary functions contains 16 functions  $f(x, y)$ :

- 1 2 constants: 0, 1
- 2 4 degenerate functions:  $x, \bar{x}, y, \bar{y}$ .
- 3 2 XOR-type functions:  $x \oplus y \oplus a$ , where  $a \in \{0, 1\}$ .

# AND-type Gates vs XOR-type Gates

## Binary functions

The set  $B_2$  of all binary functions contains 16 functions  $f(x, y)$ :

- 1 2 constants: 0, 1
- 2 4 degenerate functions:  $x, \bar{x}, y, \bar{y}$ .
- 3 2 XOR-type functions:  $x \oplus y \oplus a$ , where  $a \in \{0, 1\}$ .
- 4 8 AND-type functions:  $(x \oplus a)(y \oplus b) \oplus c$ , where  $a, b, c \in \{0, 1\}$ .

# AND-type Gates vs XOR-type Gates

## Binary functions

The set  $B_2$  of all binary functions contains 16 functions  $f(x, y)$ :

- 1 2 constants:  $0, 1$
- 2 4 degenerate functions:  $x, \bar{x}, y, \bar{y}$ .
- 3 2 XOR-type functions:  $x \oplus y \oplus a$ , where  $a \in \{0, 1\}$ .
- 4 8 AND-type functions:  $(x \oplus a)(y \oplus b) \oplus c$ , where  $a, b, c \in \{0, 1\}$ .

## Remark

Optimal circuits contain AND- and XOR-type gates **only**, as constant and degenerate gates can be easily eliminated.

# AND-type Gates vs XOR-type Gates

AND-type Gates vs XOR-type Gates

# AND-type Gates vs XOR-type Gates

## AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.

# AND-type Gates vs XOR-type Gates

## AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**

# AND-type Gates vs XOR-type Gates

## AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**
- While by assigning any constant to  $x_i$ , we obtain from  $Q(x_i, x_j) = x_i \oplus x_j \oplus c$  either  $x_j$  or  $\bar{x}_j$ .

# AND-type Gates vs XOR-type Gates

## AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**
- While by assigning any constant to  $x_i$ , we obtain from  $Q(x_i, x_j) = x_i \oplus x_j \oplus c$  either  $x_j$  or  $\bar{x}_j$ .
- This is why, in particular, the current record bounds for circuits over  $U_2 = B_2 \setminus \{\oplus, \equiv\}$  are stronger than the bounds over  $B_2$ .

# AND-type Gates vs XOR-type Gates

## AND-type Gates vs XOR-type Gates

- AND-type gates are easier to handle than XOR-type gates.
- Let  $Q(x_i, x_j) = (x_i \oplus a)(x_j \oplus b) \oplus c$  be an AND-type gate. Then by assigning  $x_i = a$  or  $x_j = b$  we make this gate constant. That is, **we eliminate not only this gate, but also all its direct successors!**
- While by assigning any constant to  $x_i$ , we obtain from  $Q(x_i, x_j) = x_i \oplus x_j \oplus c$  either  $x_j$  or  $\bar{x}_j$ .
- This is why, in particular, the current record bounds for circuits over  $U_2 = B_2 \setminus \{\oplus, \equiv\}$  are stronger than the bounds over  $B_2$ .
- Usually, the main bottleneck of a proof based on gate elimination is a circuit whose top contains many XOR-type gates.

# Multiplicative Complexity of Boolean Functions

# Multiplicative Complexity of Boolean Functions

- The minimal possible number of AND-type gates in a circuit computing  $f$  is called **the multiplicative complexity of  $f$** .

# Multiplicative Complexity of Boolean Functions

- The minimal possible number of AND-type gates in a circuit computing  $f$  is called **the multiplicative complexity of  $f$** .
- The multiplicative complexity of almost all Boolean function is about  $2^{n/2}$ .

# Multiplicative Complexity of Boolean Functions

- The minimal possible number of AND-type gates in a circuit computing  $f$  is called **the multiplicative complexity of  $f$** .
- The multiplicative complexity of almost all Boolean function is about  $2^{n/2}$ .
- The best known lower bound is  $n - 1$  (holds even for the conjunction of  $n$  variables).

# Polynomials over $\text{GF}(2)$

Polynomials over  $\text{GF}(2)$

# Polynomials over $\text{GF}(2)$

## Polynomials over $\text{GF}(2)$

- Let  $\tau(f)$  denote the unique polynomial over  $\text{GF}(2)$  representing  $f$ .

# Polynomials over $\text{GF}(2)$

## Polynomials over $\text{GF}(2)$

- Let  $\tau(f)$  denote the unique polynomial over  $\text{GF}(2)$  representing  $f$ .
- E.g.,  $\tau(\text{MOD}_{3,0}^3) = x_1x_2x_3 \oplus (1 \oplus x_1)(1 \oplus x_2)(1 \oplus x_3)$ .

# Polynomials over $\text{GF}(2)$

## Polynomials over $\text{GF}(2)$

- Let  $\tau(f)$  denote the unique polynomial over  $\text{GF}(2)$  representing  $f$ .
- E.g.,  $\tau(\text{MOD}_{3,0}^3) = x_1x_2x_3 \oplus (1 \oplus x_1)(1 \oplus x_2)(1 \oplus x_3)$ .
- Note that  $\tau(f)$  is multi-linear.

# Polynomials over $\text{GF}(2)$

## Polynomials over $\text{GF}(2)$

- Let  $\tau(f)$  denote the unique polynomial over  $\text{GF}(2)$  representing  $f$ .
- E.g.,  $\tau(\text{MOD}_{3,0}^3) = x_1x_2x_3 \oplus (1 \oplus x_1)(1 \oplus x_2)(1 \oplus x_3)$ .
- Note that  $\tau(f)$  is multi-linear.

## Lemma (Degree lower bound)

*Any circuit computing  $f$  contains at least  $\deg(\tau(f)) - 1$  AND-type gates.*

# Proof of the Degree Lower Bound

# Proof of the Degree Lower Bound

- We show that a circuit with  $d$  AND-type gates cannot compute a function of degree more than  $d + 1$  by induction.

# Proof of the Degree Lower Bound

- We show that a circuit with  $d$  AND-type gates cannot compute a function of degree more than  $d + 1$  by induction.
- Note that it is important that we are working in  $\text{GF}(2)$ . To compute  $x^k$  one needs only about  $\log k$  binary multiplications.

# Proof of the Degree Lower Bound

- We show that a circuit with  $d$  AND-type gates cannot compute a function of degree more than  $d + 1$  by induction.
- Note that it is important that we are working in  $\text{GF}(2)$ . To compute  $x^k$  one needs only about  $\log k$  binary multiplications.
- Consider the first (in a topological sorting of all the gates) AND-type gate. Note that it computes a function of degree at most 2.

# Proof of the Degree Lower Bound

- We show that a circuit with  $d$  AND-type gates cannot compute a function of degree more than  $d + 1$  by induction.
- Note that it is important that we are working in  $\text{GF}(2)$ . To compute  $x^k$  one needs only about  $\log k$  binary multiplications.
- Consider the first (in a topological sorting of all the gates) AND-type gate. Note that it computes a function of degree at most 2.
- Replace this gate by a new variable. We now have a circuit with  $d - 1$  AND-type gates and hence, by induction, it computes a function of degree at most  $d$ .

# Proof of the Degree Lower Bound

- We show that a circuit with  $d$  AND-type gates cannot compute a function of degree more than  $d + 1$  by induction.
- Note that it is important that we are working in  $\text{GF}(2)$ . To compute  $x^k$  one needs only about  $\log k$  binary multiplications.
- Consider the first (in a topological sorting of all the gates) AND-type gate. Note that it computes a function of degree at most 2.
- Replace this gate by a new variable. We now have a circuit with  $d - 1$  AND-type gates and hence, by induction, it computes a function of degree at most  $d$ .
- Now return back the removed gate. Since we are in  $\text{GF}(2)$ , this increases the degree by at most 1. □

# Combined Complexity Measure

## Idea

In a typical bottleneck case we usually have only XOR-type gates, however we are given several AND-type gates in advance.

# Combined Complexity Measure

## Idea

In a typical bottleneck case we usually have only XOR-type gates, however we are given several AND-type gates in advance. **Let us increase the weight of a XOR-type gate.**

# Combined Complexity Measure

## Idea

In a typical bottleneck case we usually have only XOR-type gates, however we are given several AND-type gates in advance. **Let us increase the weight of a XOR-type gate.**

## Definition

For a circuit  $C$ , let  $A(C)$  and  $X(C)$  denote the number of AND- and XOR-type gates in  $C$ , respectively. Let also  $\mu(C) = 3X(C) + 2A(C)$ .

# An Improved Lower Bound

## Lemma

*For any circuit  $C$  computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$ .*

# An Improved Lower Bound

## Lemma

For any circuit  $C$  computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$ .

## Proof

# An Improved Lower Bound

## Lemma

For any circuit  $C$  computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$ .

## Proof

- As in the previous proof, we consider a top gate  $Q(x_i, x_j)$  and assume wlog that  $x_i$  feeds also another gate  $P$ .



# An Improved Lower Bound

## Lemma

For any circuit  $C$  computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$ .
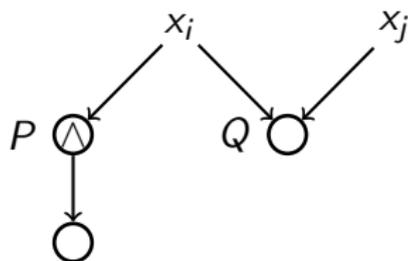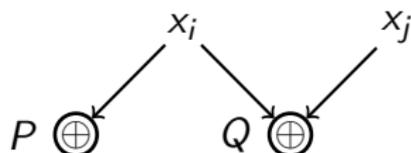
## Proof

- As in the previous proof, we consider a top gate  $Q(x_i, x_j)$  and assume wlog that  $x_i$  feeds also another gate  $P$ . There are two cases:





# An Improved Lower Bound

## Lemma

For any circuit  $C$  computing  $f \in Q_{2,3}^n$ ,  $\mu(C) = 3X(C) + 2A(C) \geq 6n - 24$ .
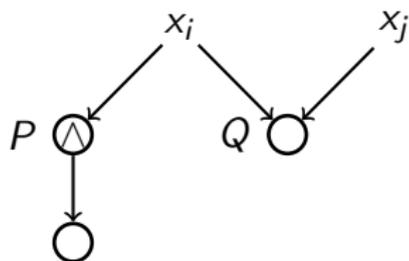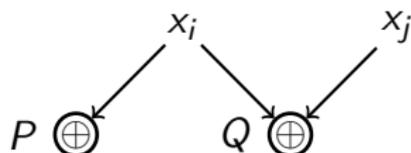
## Proof

- As in the previous proof, we consider a top gate  $Q(x_i, x_j)$  and assume wlog that  $x_i$  feeds also another gate  $P$ . There are two cases:



- In the former case, by assigning  $x_i$  a constant one eliminates both XOR-type gates. In the latter, by assigning  $x_i$  **the right constant** one eliminates  $P$ ,  $Q$  and all successors of  $P$ . In both cases,  $\mu$  is reduced by at least 6. □

## $7n/3$ Lower Bound

### Lemma

Let  $f \in Q_{2,3}^n$  and  $\deg(\tau(f)) \geq n - c$ , then  $C(f) \geq 7n/3 - c'$ .

## $7n/3$ Lower Bound

### Lemma

Let  $f \in Q_{2,3}^n$  and  $\deg(\tau(f)) \geq n - c$ , then  $C(f) \geq 7n/3 - c'$ .

### proof

Let  $C$  be an optimal circuit computing  $f$ .

## $7n/3$ Lower Bound

### Lemma

Let  $f \in Q_{2,3}^n$  and  $\deg(\tau(f)) \geq n - c$ , then  $C(f) \geq 7n/3 - c'$ .

### proof

Let  $C$  be an optimal circuit computing  $f$ .

$$\begin{array}{r} 3X(C) + 2A(C) \geq 6n - 24 \\ A(C) \geq n - c - 1 \\ \hline 3C(f) = 3X(C) + 3A(C) \geq 7n - 25 - c \end{array}$$



# Improving the Degree Lower Bound

## Improving the Degree Lower Bound

- Consider the function  $\text{MOD}_{3,2}^3$ :

$$\tau(\text{MOD}_{3,2}^3) = x_1x_2(1 \oplus x_3) \oplus x_1(1 \oplus x_2)x_3 \oplus (1 \oplus x_1)x_2x_3 =$$

# Improving the Degree Lower Bound

- Consider the function  $\text{MOD}_{3,2}^3$ :

$$\begin{aligned}\tau(\text{MOD}_{3,2}^3) &= x_1x_2(1 \oplus x_3) \oplus x_1(1 \oplus x_2)x_3 \oplus (1 \oplus x_1)x_2x_3 = \\ &= x_1x_2x_3 \oplus x_1x_2 \oplus x_2x_3 \oplus x_1x_3\end{aligned}$$

## Improving the Degree Lower Bound

- Consider the function  $\text{MOD}_{3,2}^3$ :

$$\begin{aligned}\tau(\text{MOD}_{3,2}^3) &= x_1x_2(1 \oplus x_3) \oplus x_1(1 \oplus x_2)x_3 \oplus (1 \oplus x_1)x_2x_3 = \\ &= x_1x_2x_3 \oplus x_1x_2 \oplus x_2x_3 \oplus x_1x_3\end{aligned}$$

- The Degree Lower Bound Lemma says that one needs at least two binary multiplications to compute  $\text{MOD}_{3,2}^3$ , just because  $\tau(\text{MOD}_{3,2}^3)$  contains a monomial of degree 3.

## Improving the Degree Lower Bound

- Consider the function  $\text{MOD}_{3,2}^3$ :

$$\begin{aligned}\tau(\text{MOD}_{3,2}^3) &= x_1x_2(1 \oplus x_3) \oplus x_1(1 \oplus x_2)x_3 \oplus (1 \oplus x_1)x_2x_3 = \\ &= x_1x_2x_3 \oplus x_1x_2 \oplus x_2x_3 \oplus x_1x_3\end{aligned}$$

- The Degree Lower Bound Lemma says that one needs at least two binary multiplications to compute  $\text{MOD}_{3,2}^3$ , just because  $\tau(\text{MOD}_{3,2}^3)$  contains a monomial of degree 3.
- It however contains other monomials, so probably one needs more binary multiplications in the worst case to compute  $\text{MOD}_{3,2}^3$ ?

## Improving the Degree Lower Bound

- Consider the function  $\text{MOD}_{3,2}^3$ :

$$\begin{aligned}\tau(\text{MOD}_{3,2}^3) &= x_1x_2(1 \oplus x_3) \oplus x_1(1 \oplus x_2)x_3 \oplus (1 \oplus x_1)x_2x_3 = \\ &= x_1x_2x_3 \oplus x_1x_2 \oplus x_2x_3 \oplus x_1x_3\end{aligned}$$

- The Degree Lower Bound Lemma says that one needs at least two binary multiplications to compute  $\text{MOD}_{3,2}^3$ , just because  $\tau(\text{MOD}_{3,2}^3)$  contains a monomial of degree 3.
- It however contains other monomials, so probably one needs more binary multiplications in the worst case to compute  $\text{MOD}_{3,2}^3$ ?
- No, two multiplications are enough:

$$\tau(\text{MOD}_{3,2}^3) = (x_1 \oplus x_2 \oplus x_1x_2)(x_1 \oplus x_2 \oplus x_3 \oplus 1).$$

## Improving the Degree Lower Bound

- Consider the function  $\text{MOD}_{3,2}^3$ :

$$\begin{aligned}\tau(\text{MOD}_{3,2}^3) &= x_1x_2(1 \oplus x_3) \oplus x_1(1 \oplus x_2)x_3 \oplus (1 \oplus x_1)x_2x_3 = \\ &= x_1x_2x_3 \oplus x_1x_2 \oplus x_2x_3 \oplus x_1x_3\end{aligned}$$

- The Degree Lower Bound Lemma says that one needs at least two binary multiplications to compute  $\text{MOD}_{3,2}^3$ , just because  $\tau(\text{MOD}_{3,2}^3)$  contains a monomial of degree 3.
- It however contains other monomials, so probably one needs more binary multiplications in the worst case to compute  $\text{MOD}_{3,2}^3$ ?
- No, two multiplications are enough:

$$\tau(\text{MOD}_{3,2}^3) = (x_1 \oplus x_2 \oplus x_1x_2)(x_1 \oplus x_2 \oplus x_3 \oplus 1).$$

- Moreover, the multiplicative complexity of any symmetric function is at most  $n + o(n)$  [Boyar, Peralta, Pochuev, 2000].

# Open Problems

# Open Problems

- 1 Improve the lower bounds  $3n - o(n)$  and  $5n - o(n)$  for the circuit complexity over  $B_2$  and  $U_2$ , respectively.

# Open Problems

- 1 Improve the lower bounds  $3n - o(n)$  and  $5n - o(n)$  for the circuit complexity over  $B_2$  and  $U_2$ , respectively.
- 2 Close the gaps:

$$2.5n \leq C_{B_2}(\text{MOD}_3^n) \leq 3n$$

$$4n \leq C_{U_2}(\text{MOD}_4^n) \leq 5n$$

# Open Problems

- 1 Improve the lower bounds  $3n - o(n)$  and  $5n - o(n)$  for the circuit complexity over  $B_2$  and  $U_2$ , respectively.
- 2 Close the gaps:

$$2.5n \leq C_{B_2}(\text{MOD}_3^n) \leq 3n$$

$$4n \leq C_{U_2}(\text{MOD}_4^n) \leq 5n$$

- 3 Prove a  $cn$  lower bound (for a constant  $c > 1$ ) on the multiplicative complexity of an explicit Boolean function.

**Thank you for your attention!**